

Attempt in all questions and assume any missing data.

**Q1-** Draw the following logic circuits, explain its operations, and write its truth table:

- 1- Active-low S-R latch
- 2- Gated S-R latch.
- 3- Positive edge triggered D flip flop.
- 4- Negative edge triggered J-K flip flop with asynchronous reset and clear inputs.

**Q2:-(a):-** Design a frequency divider circuit using a J-K positive edge triggered flip flop. Input waveform has a frequency 16 k Hz, and the output waveform has a frequency 1 k Hz.

**(b):-** For a negative edge-triggered J-K flip-flop with the inputs shown in Figure 1, develop the Q output waveform relative to the clock. Assume that Q is initially LOW.

 


Figure (1)

**Q3-** Design the following counters:

- 1- A 3-bit asynchronous binary counter with timing diagram.
- 2- A 4-bit synchronous counter with timing diagram.
- 3- A synchronous BCD counter.
- 4- A 3-bit up/down synchronous binary counter.

**Q4-** Implement the decoding of binary state 2 and binary state 7 of a 3-bit synchronous counter. Show the entire counter timing diagram and the output waveforms of the decoding gates.

**Q5-** Design the following shift registers:

- 1- Serial in/Parallel out.
- 2- Parallel in/Serial out.
- 3- Bidirectional.
- 4- Serial in/Serial out.

Q6- Serial data transmission from one digital system to another is commonly used to reduce the number of wires in the transmission line. Design a serial-to-parallel data converter to solve this problem for the serial data format shown in Figure (3).



Figure (3)

Q7- (a): Draw the block diagram of a 3-dimensional RAM memory showing address bus, address decoders, bidirectional data bus, and read/write inputs. Explain the function of each component.

(b): Explain with drawing the following basic operation of the DRAM:

- (1)-Writing a 1 into the memory cell.
- (2)-Writing a 0 to memory cell.
- (3)-Reading a 1 from the memory cell.
- (4)-Refreshing a stored 1.